


# *What Is Verilog?*

---

- Hardware Description Language (HDL)
  - Not a *programming* language! (more on this later)
- Describes digital systems
  - Behavioral
  - Structural
- How is this useful?
  - Can't draw gate-level schematics of complex systems – big mess
  - Gate-level simulation unnecessarily slow
  - HDLs faster to simulate, and still provide:
    - Synthesizable low-level implementation
    - Hardware concurrency
    - Ease of use



# Synthesizable?

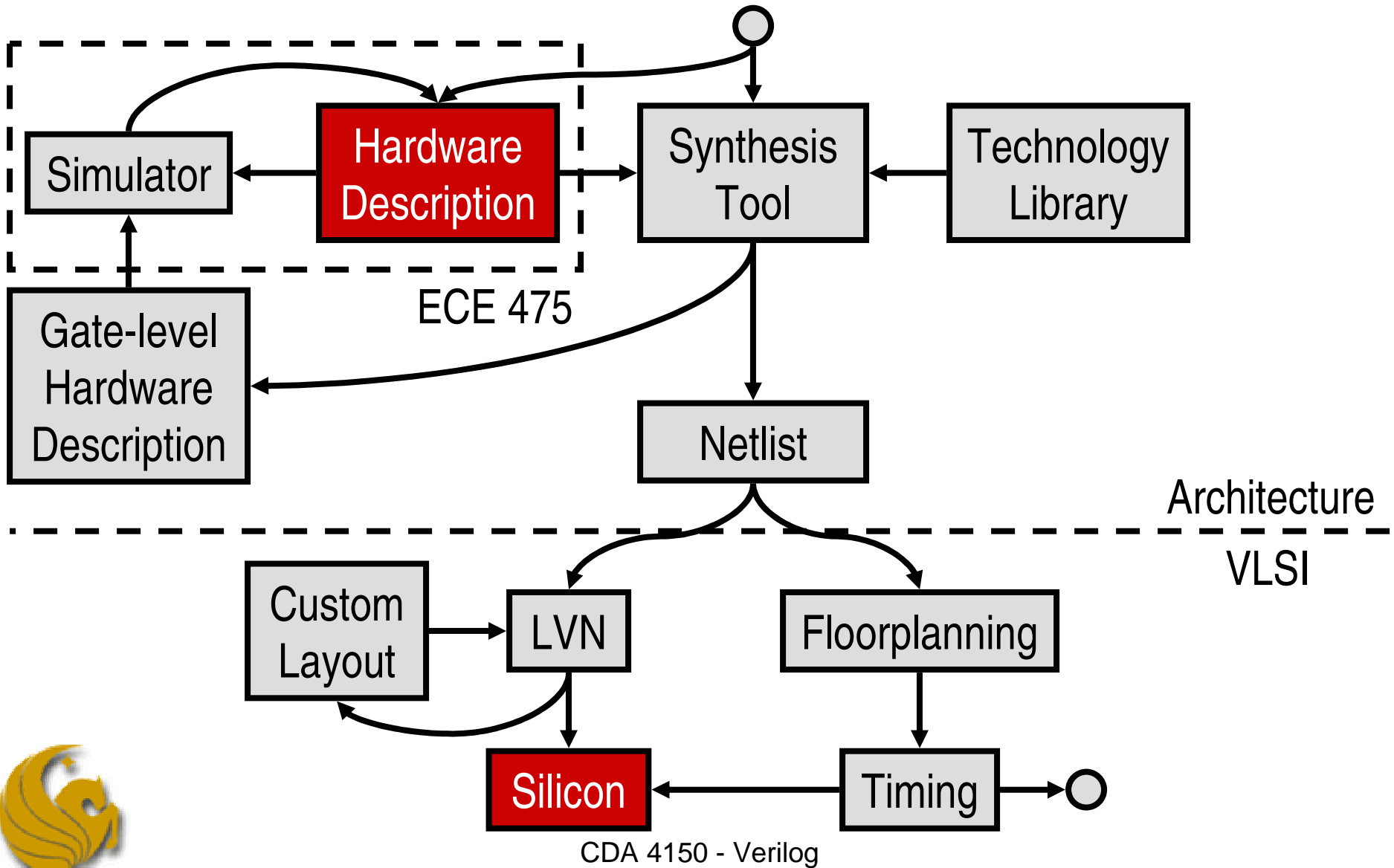

# *Verilog vs. VHDL*

---

- VHDL (VHSIC HDL)
  - ADA-like syntax (ADA anyone?)
  - Older, less expressive
- Verilog
  - C-like syntax (C anyone?)
  - Larger user community
  - Not VHDL



# *HDL vs. Programming Language*

---



## **NOT A PROGRAMMING LANGUAGE**

- Repeat on every keystroke: “I’m... designing... hardware...”
- No variables (outlawed) – signals!
  - Regs (containers)
  - Wires (connections)
- HDLs concurrent
  - Which happens first?  
`assign a = ~b;`  
`assign c = d;`
- Operators do not come for free – actual hardware!
  - Use ‘+’, ‘-’, ‘<<’ sparingly; never use ‘\*’, ‘/’



 
 
# NAND Gate, Behavioral

```
module NAND(a,b,out);  
input a;  
input b;  
output out;  
  
    assign out = ~(a&b);  
endmodule
```



 
 
# AND Gate, Behavioral

```
module AND(x,y,out);  
input x;  
input y;  
output out;  
  
    assign out = x&y;  
endmodule
```


  
# AND Gate, Structural

```
module AND(x,y,out);  
input x;  
input y;  
output out;  
wire z;  
  
    NAND MyNAND(.a(x),.b(y),.out(z));  
    assign out = ~z;  
endmodule
```



# Combinational Logic

---

- Done using *assign* statements
- LHS must be declared *wire*
  - Cannot feed into *reg* – it's combinational!
- Typical operators
  - '&', '|', '^', '~', instantiate corresponding gates
  - '==', '!=', instantiate comparators, return one bit
  - Physical data types: '0', '1', 'x' ("don't care"), 'z' ("high impedance")

```
assign s = a^b^ci;  
assign co = a&b|a&ci|b&ci;
```

(What does this do?)





# Buses

---

- Can actually operate on multiple bits in parallel
  - Correspondingly more hardware, of course
  - Default bit width is 1

```
module AND(x,y,out);  
input x;  
input y;  
output out;
```

```
    assign out = x&y;  
endmodule
```

```
module AND8(x,y,out);  
input [7:0] x;  
input [7:0] y;  
output [7:0] out;
```

```
    assign out = x&y;  
endmodule
```



# Concatenation, Repetition

---

- Syntax:  $R\{E1, E2, \dots, En\}$ 
  - $R$  repetitions (default 1) of the concatenation of  $E1, E2, \dots, En$


```
reg[15:0] a;  
reg[31:0] b;  
wire[31:0] out;  
  
assign out = {16{a[15]}, a}+b;
```

(What does this do?)


 
# Sequential Logic

- Finite State Machines (CDA 3103 anyone?)



- Need event-driven simulation capability
- Need to trigger on edge – not value

(What is this?)



# Sequential Logic

---

```
module DFF(d,q,clk);  
  input clk;  
  input d;  
  output q;  
  reg q;  
  
  always @(posedge clk) begin  
    q <= `TICK d;  
  end  
endmodule
```

- Can be *negedge* as well (and *clk* any other name)
- ``define TICK #2` (two Verilog time units) – *clk* period should be  $\gg 2$
- ``TICK q <= d;` – Legal! Wrong!



# Sequential Logic

- Always use nonblocking assignment '`<=`' in sequential *always* blocks
- Always use '`TICK`' before RHS in sequential *always* blocks
- Clock only signal in sensitivity list
- LHS must be declared *reg*
  - cannot use *wire* – it's sequential logic!
- Hoist combinational logic outside of *always* blocks as much as possible

```
...  
always @(posedge clk) begin  
    q <= `TICK a&(32{b==c});  
end
```

Legal

```
wire[31:0] d;  
assign d = a&(32{b==c});  
...  
always @(posedge clk) begin  
    q <= `TICK d;  
end
```

Preferred



# Control Flow

---

- Can be used in *always* blocks
- Instantiates actual mux – not programming!

```
module DFF(d,r,q,clk);  
input clk; input d; input r;  
output q;  
reg q;  
  
    always @(posedge clk) begin  
        if(r == 1'b1) begin  
            q <= `TICK 1'b0;  
        end  
        else begin  
            q <= `TICK d;  
        end  
    end  
endmodule
```

(What does this do?)



# *Combinational always Blocks*

---

- Useful for complex combinational logic
- All RHS signals must appear on sensitivity list
- LHS must be assigned in every possible case
  - otherwise implied sequential logic!

```
always @(sel or a) begin
    if(sel == 2'b0) begin
        z = 1'b0;
    end
    else if(sel == 2'b1) begin
        z = a;
    end
end
```

(What does this do? Is it correct?)



# Extra Hardware?

---

- Watch out for “programming” too much hardware
  - Fortunately synthesis tool (somewhat) smart – but don’t count on it

```
always @(posedge clk) begin
  if(i) begin
    x <= `TICK a+b;
  end
  else if(j) begin
    y <= `TICK a+b;
  end
  else begin
    z <= `TICK a+b;
  end
end
```

(What is the generated hardware?)





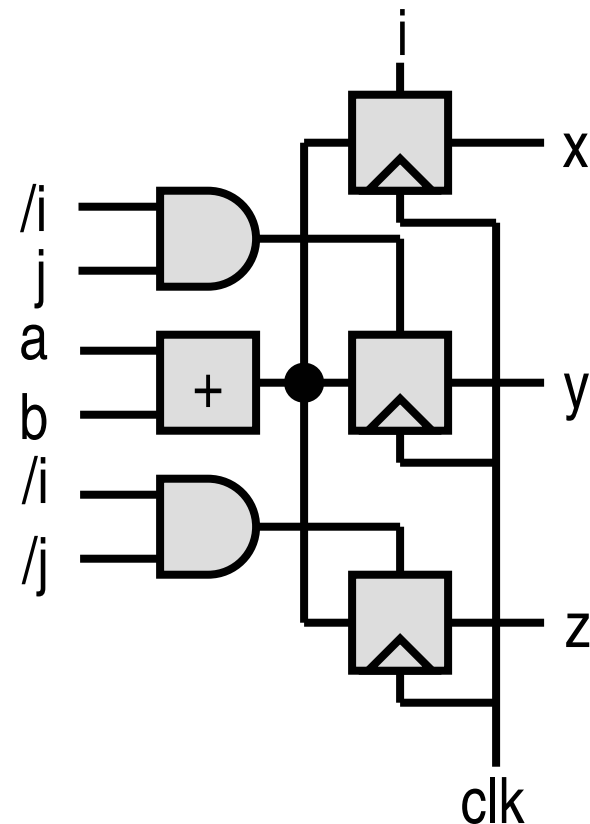
# Extra Hardware?

- Watch out for “programming” too much hardware
  - Fortunately synthesis tool (somewhat) smart – but don’t count on it

```
always @(posedge clk) begin
  if(i) begin
    x <= `TICK a+b;
  end
  else if(j) begin
    y <= `TICK a+b;
  end
  else begin
    z <= `TICK a+b;
  end
end
```



# *Verilog Is Not C!*

---

- Verilog is concurrent, C is not

```
initial begin
    a = 1'b0;
    b = 1'b0;
end
```

```
always @(posedge clk) begin
    a <= `TICK 1'b1;
    b <= `TICK a;
end
```

(Value of *a* and *b* after clock tick?)




# Other Useful Hardware Structures

- Register files/memories

```
reg[31:0] regfile[0:7];
```

```
wire[31:0] reg2;  
wire r2b4;
```

 
```
assign reg2 = regfile[2];  
assign r2b4 = reg2[4];
```


 
# Other Useful Hardware Structures

- Tri-state devices

```
reg[31:0] mem[0:7];  
wire[31:0] a;  
wire[31:0] d;  
wire rd;  
  
assign d = rd?mem[a]:32'bz;
```



What is this?



# *Last Remarks*

---

- It often helps to draw hardware diagrams first
- If stuck, think about what hardware does
- Use `make clobber` to clean up, or force a re-compile
- Use `vcheck!` (`vcheck *.v`)

