

Principles of Computer Architecture

Miles Murdocca and Vincent Heuring

Chapter 6: Datapath and Control

Chapter Contents

6.1 Basics of the Microarchitecture

6.2 A Microarchitecture for the ARC

6.3 Hardwired Control


6.4 Case Study: The VHDL Hardware Description Language

The Fetch-Execute Cycle

- **The steps that the control unit carries out in executing a program are:**
 - (1) Fetch the next instruction to be executed from memory.**
 - (2) Decode the opcode.**
 - (3) Read operand(s) from main memory, if any.**
 - (4) Execute the instruction and store results.**
 - (5) Go to step 1.**

High Level View of Microarchitecture

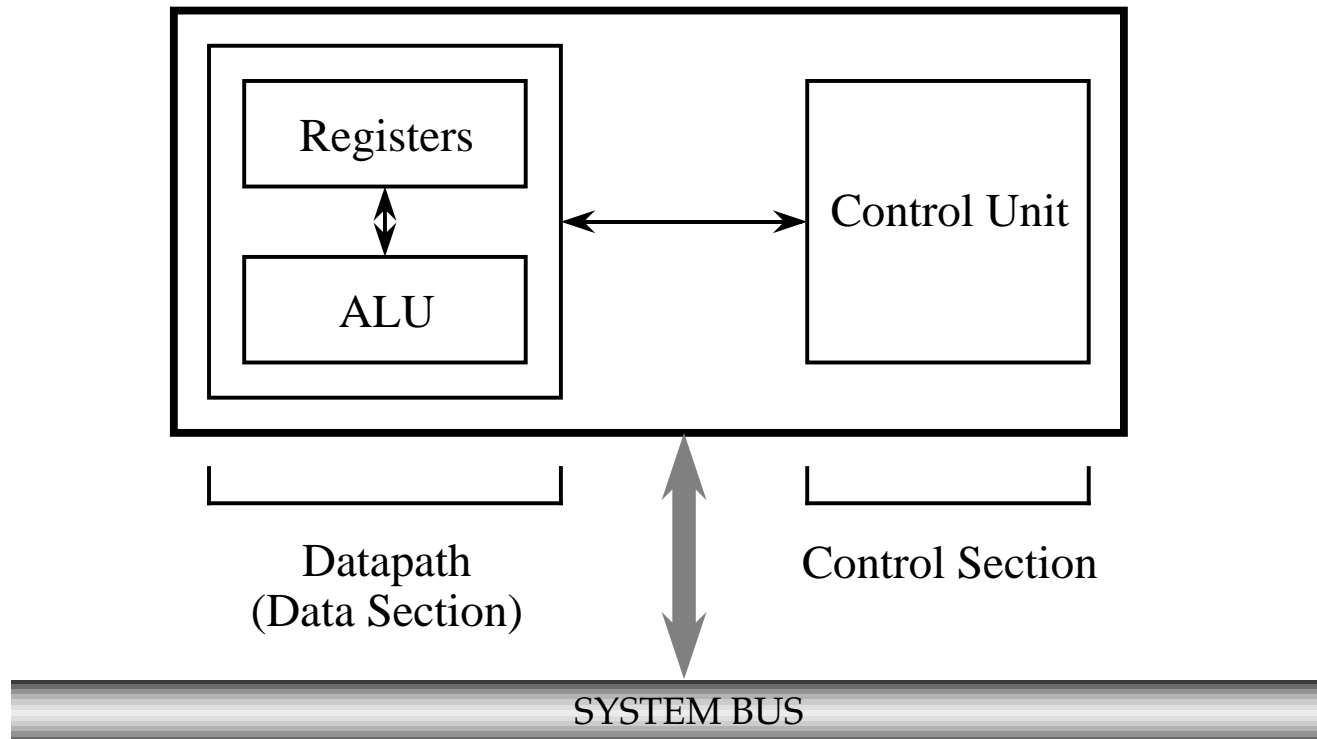
- The microarchitecture consists of the control unit and the programmer-visible registers, functional units such as the ALU, and any additional registers that may be required by the control unit.



ARC Instruction Subset

	Mnemonic	Meaning
Memory	ld	Load a register from memory
	st	Store a register into memory
Logic	sethi	Load the 22 most significant bits of a register
	andcc	Bitwise logical AND
	orcc	Bitwise logical OR
	orncc	Bitwise logical NOR
	srl	Shift right (logical)
Arithmetic	addcc	Add
	call	Call subroutine
Control	jmp1	Jump and link (return from subroutine call)
	be	Branch if equal
	bneg	Branch if negative
	bcs	Branch on carry
	bvs	Branch on overflow
	ba	Branch always

ARC Instruction Formats

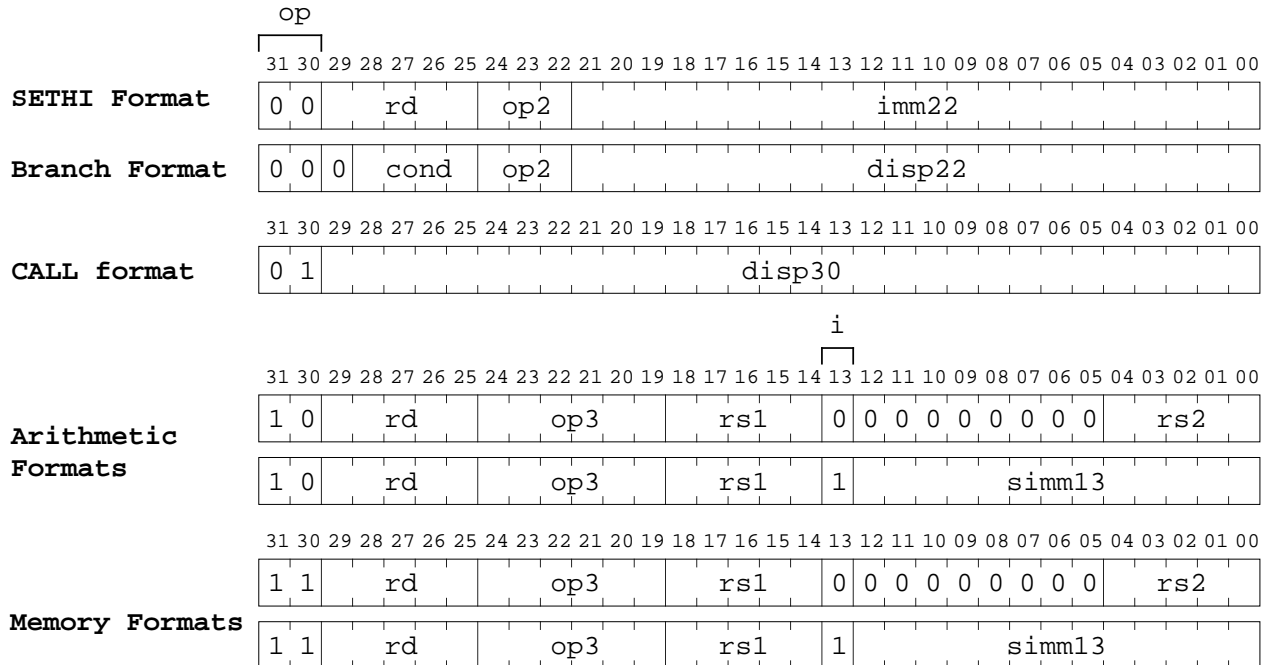


op	Format
00	SETHI/Branch
01	CALL
10	Arithmetic
11	Memory

op2	Inst.
010	branch
100	sethi


op3 (op=10)
010000 addcc
010001 andcc
010010 orcc
010110 orncc
100110 srl
111000 jmp1

op3 (op=11)
000000 ld
000100 st

cond	branch
0001	be
0101	bcs
0110	bneg
0111	bvs
1000	ba

 


ARC Datapath

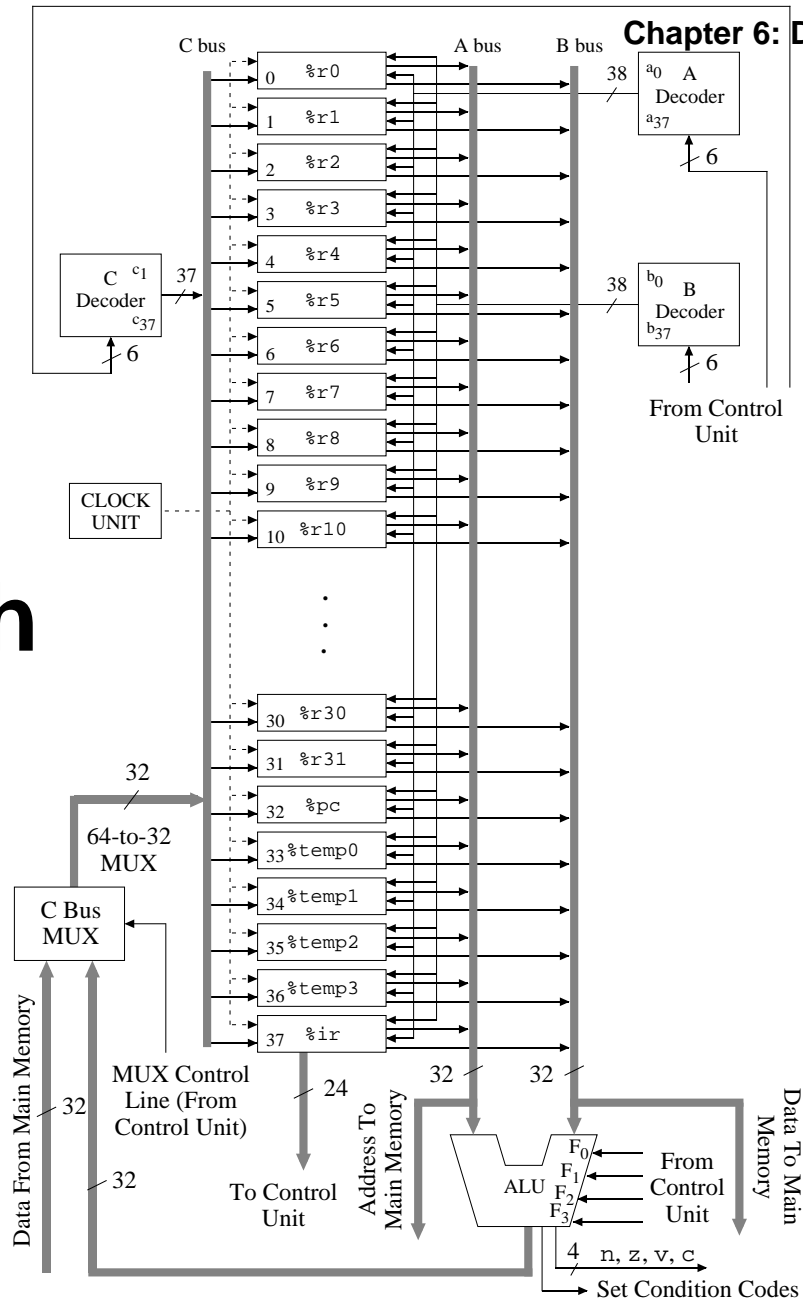

ARC ALU Operations

F_3 F_2 F_1 F_0	Operation	Changes Condition Codes
0 0 0 0	ANDCC (A, B)	yes
0 0 0 1	ORCC (A, B)	yes
0 0 1 0	NORCC (A, B)	yes
0 0 1 1	ADDCC (A, B)	yes
0 1 0 0	SRL (A, B)	no
0 1 0 1	AND (A, B)	no
0 1 1 0	OR (A, B)	no
0 1 1 1	NOR (A, B)	no
1 0 0 0	ADD (A, B)	no
1 0 0 1	LSHIFT2 (A)	no
1 0 1 0	LSHIFT10 (A)	no
1 0 1 1	SIMM13 (A)	no
1 1 0 0	SEXT13 (A)	no
1 1 0 1	INC (A)	no
1 1 1 0	INCPC (A)	no
1 1 1 1	RSHIFT5 (A)	no


Gate-Level Layout of Barrel Shifter

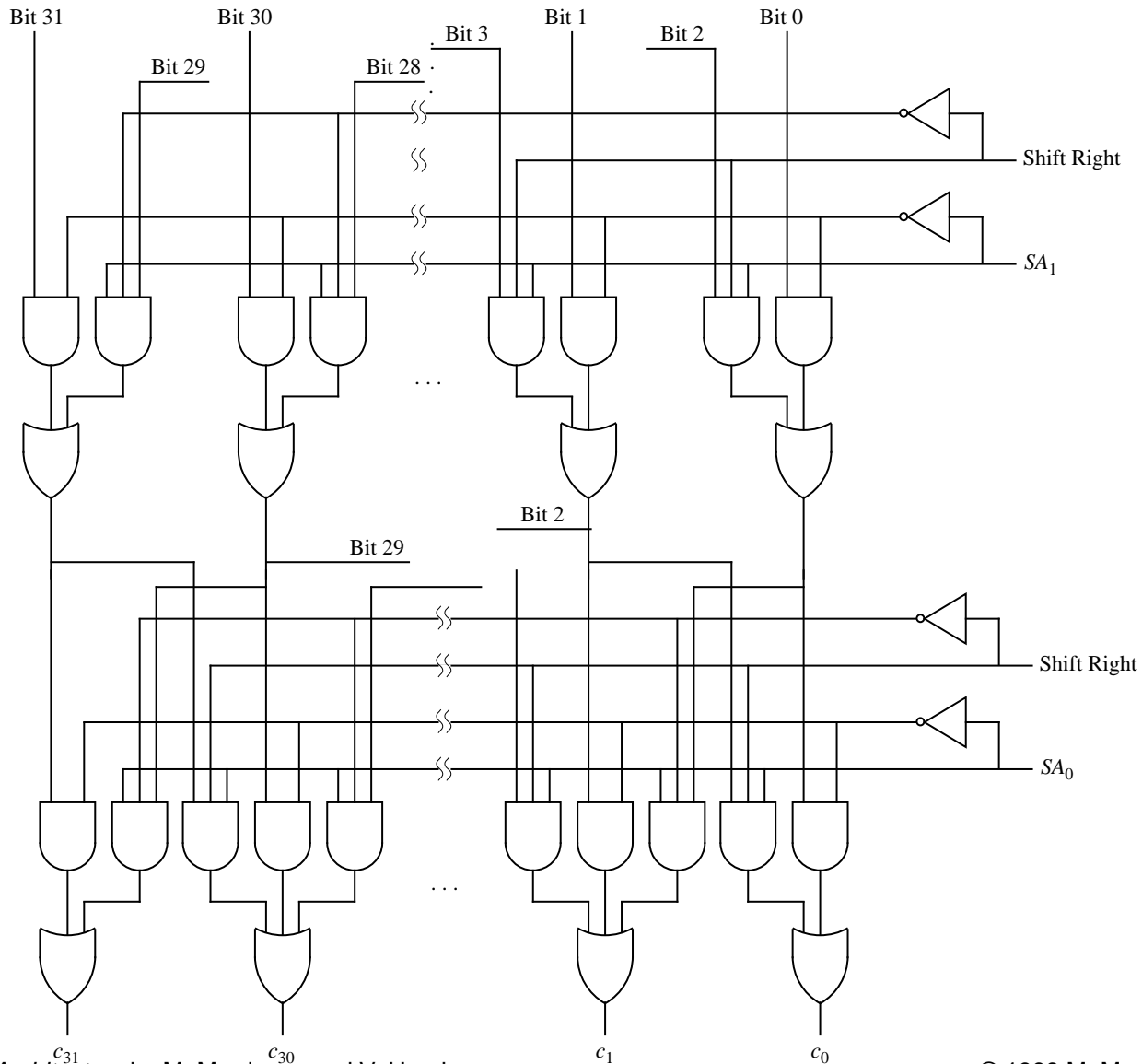


Truth Table for (Most of the) ALU LUTs

	F_3	F_2	F_1	F_0	Carry <i>In</i>	a_i	b_i	z_i	Carry <i>Out</i>
ANDCC	0	0	0	0	0	0	0	0	0
	0	0	0	0	0	0	1	0	0
	0	0	0	0	0	1	0	0	0
	0	0	0	0	0	1	1	1	0
	0	0	0	0	1	0	0	0	0
	0	0	0	0	1	0	1	0	0
	0	0	0	0	1	1	0	0	0
	0	0	0	0	1	1	1	1	0
ORCC	0	0	0	1	0	0	0	0	0
	0	0	0	1	0	0	1	1	0
	0	0	0	1	0	1	0	1	0
	0	0	0	1	0	1	1	1	0
	0	0	0	1	1	0	0	0	0
	0	0	0	1	1	0	1	1	0
					.				.
					.				.
				.				.	


Design of Register %r1

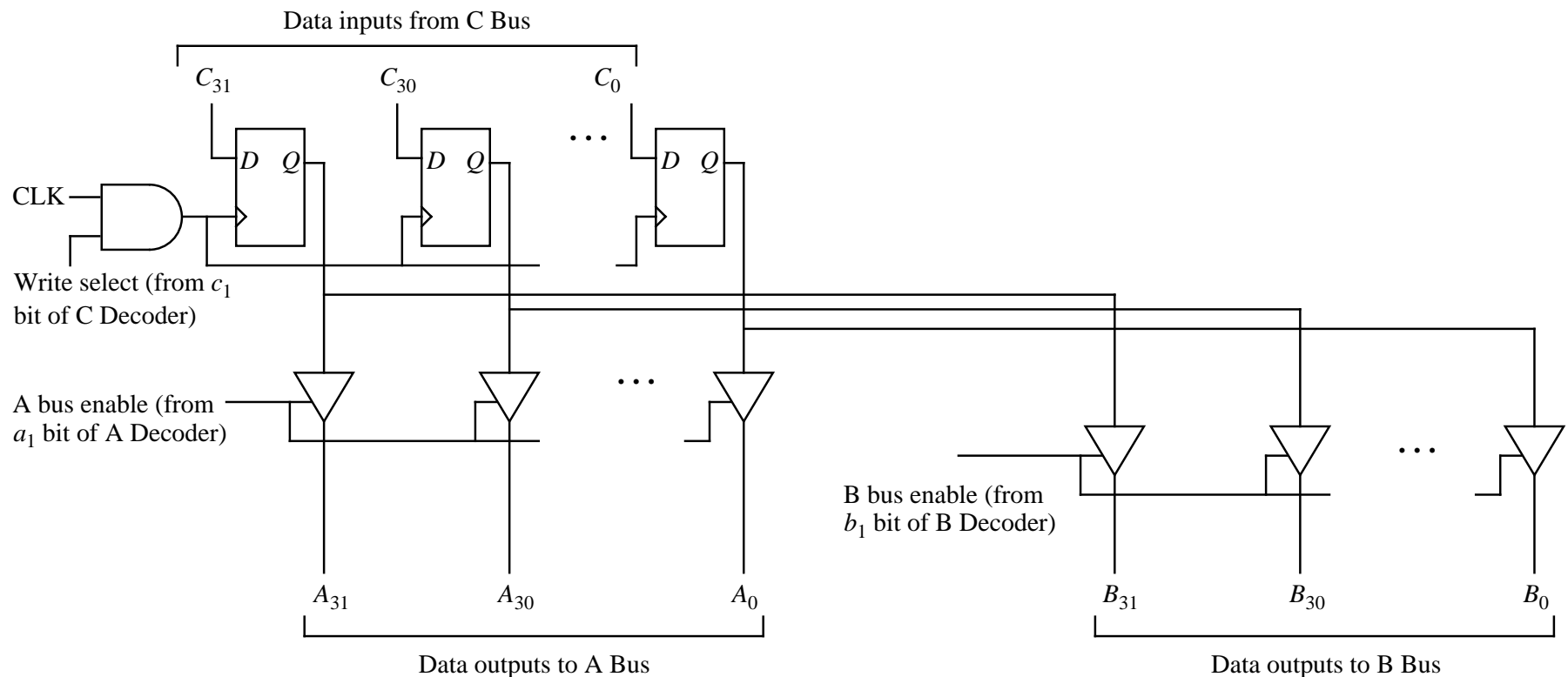

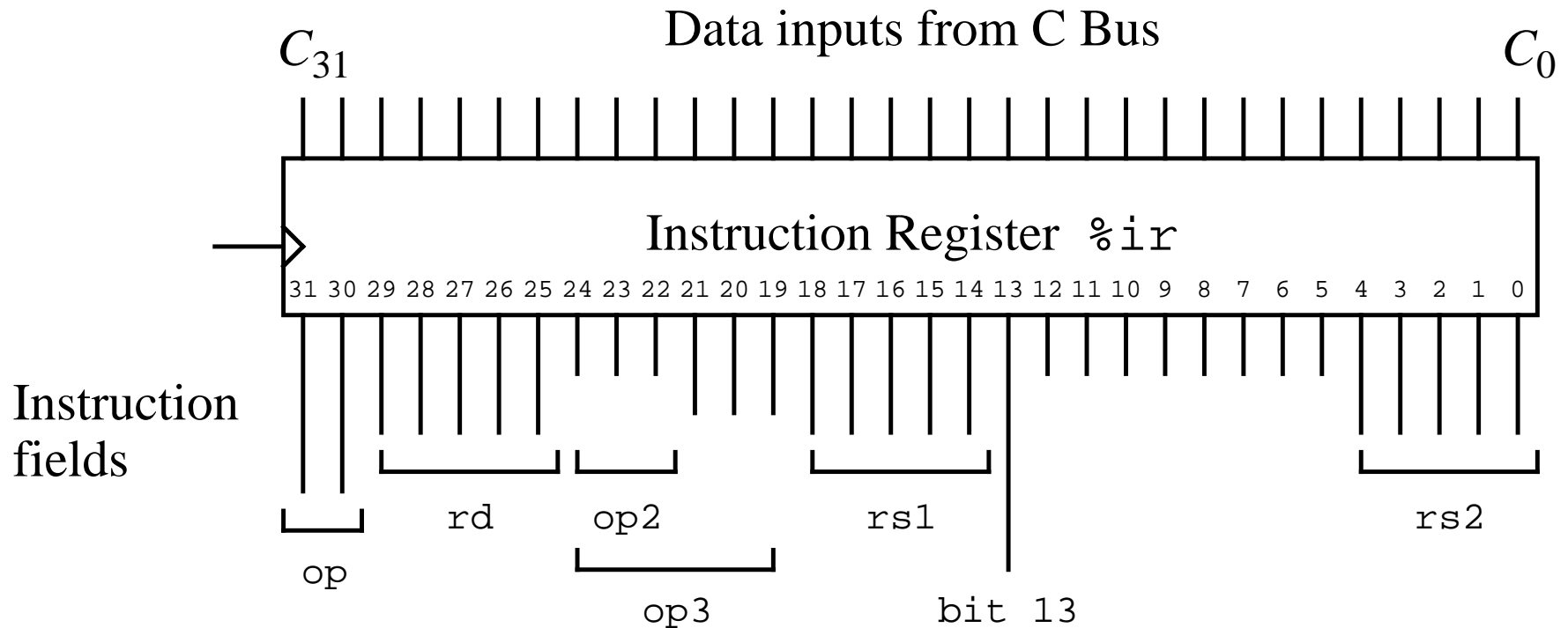
Outputs to Control Unit from Register %ir



Microarchitecture of the ARC

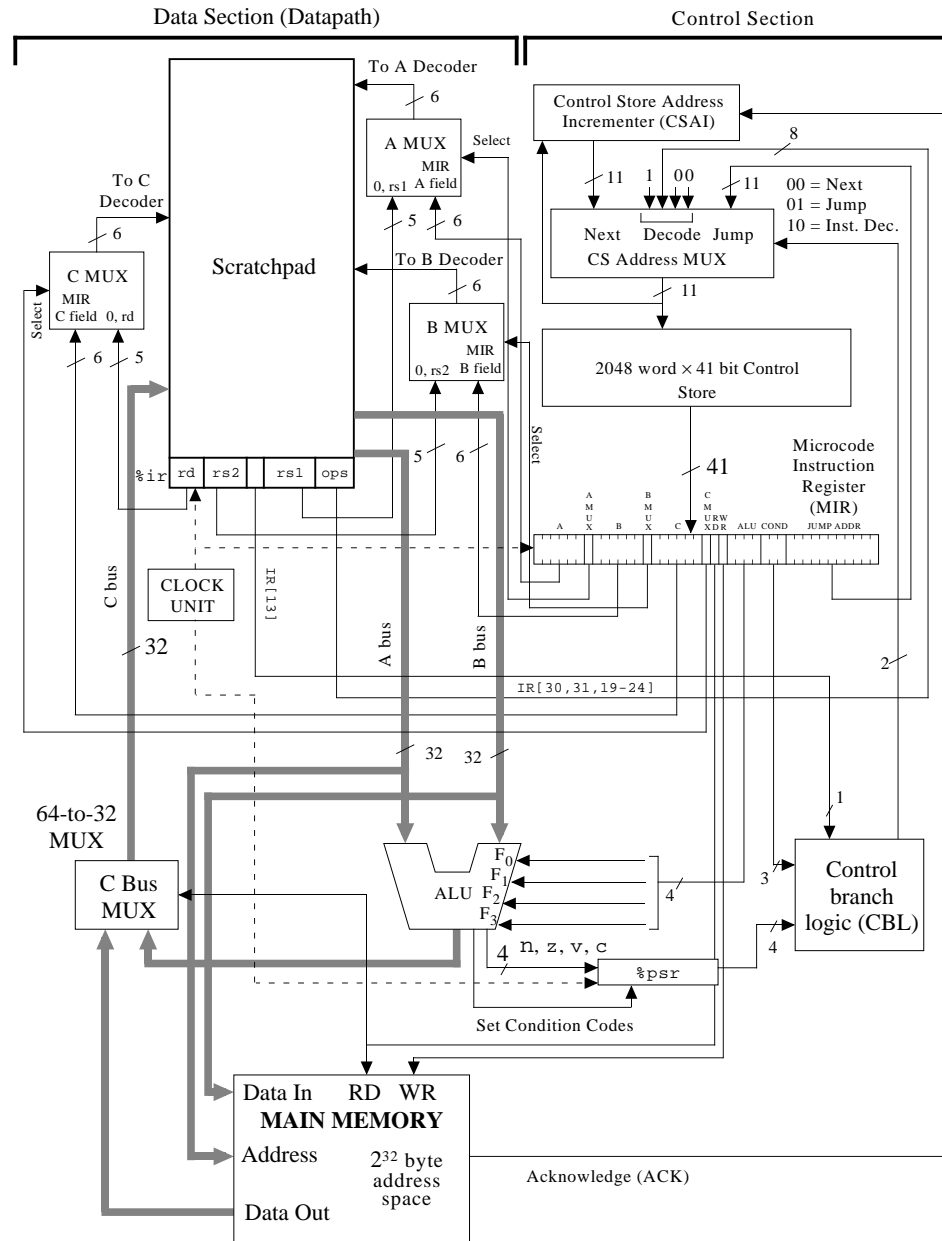


Microword Format

 


Settings for the COND Field of the Microword

C_2	C_1	C_0	Operation
0	0	0	Use NEXT ADDR
0	0	1	Use JUMP ADDR if $n = 1$
0	1	0	Use JUMP ADDR if $z = 1$
0	1	1	Use JUMP ADDR if $v = 1$
1	0	0	Use JUMP ADDR if $c = 1$
1	0	1	Use JUMP ADDR if $IR[13] = 1$
1	1	0	Use JUMP ADDR
1	1	1	DECODE

 DECODE Format for Microinstruction Address



Timing Relationships for the Registers

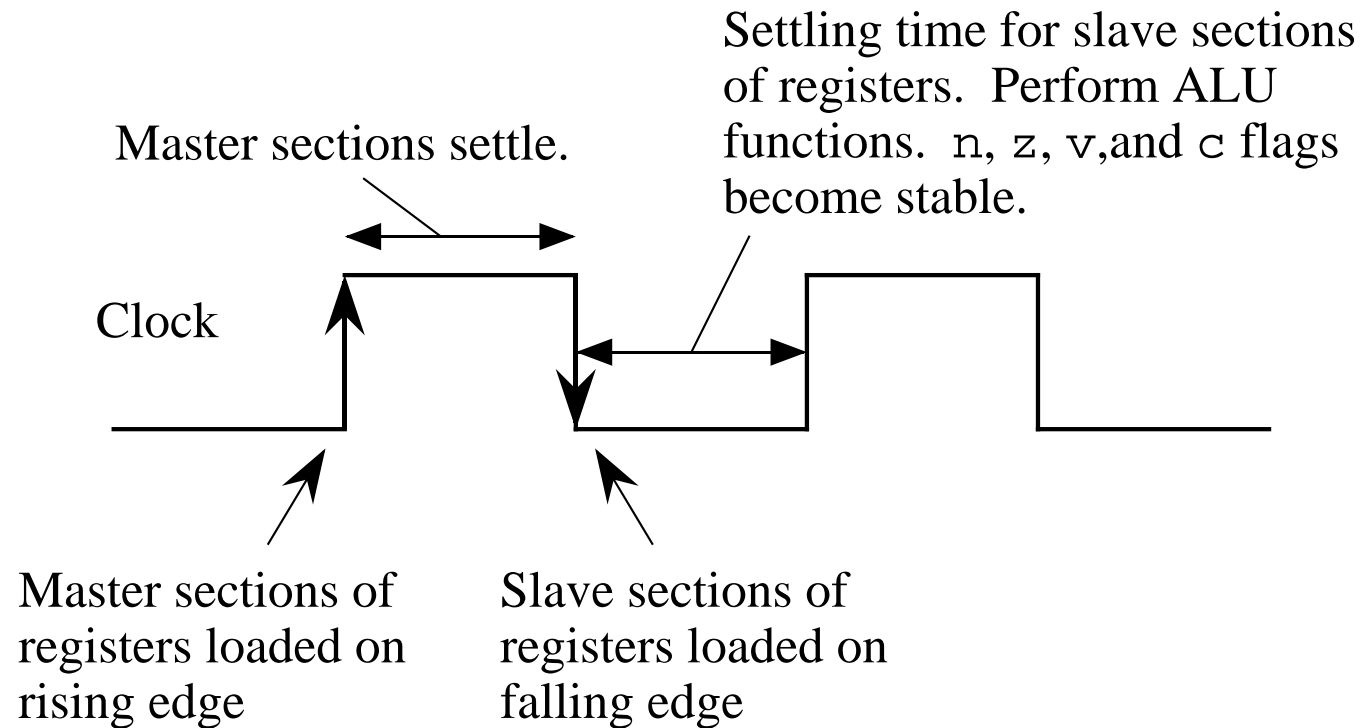

Partial ARC Microprogram

Address	Operation Statements	Comment
	0: R[ir] ← AND(R[pc],R[pc]); READ;	/ Read an ARC instruction from main memory
	1: DECODE;	/ 256-way jump according to opcode
	/ sethi	
1152:	R[rd] ← LSHIFT10(ir); GOTO 2047;	/ Copy imm22 field to target register
	/ call	
1280:	R[15] ← AND(R[pc],R[pc]);	/ Save %pc in %r15
1281:	R[temp0] ← ADD(R[ir],R[ir]);	/ Shift disp30 field left
1282:	R[temp0] ← ADD(R[temp0],R[temp0]);	/ Shift again
1283:	R[pc] ← ADD(R[pc],R[temp0]);	/ Jump to subroutine
	GOTO 0;	
	/ addcc	
1600:	IF R[IR[13]] THEN GOTO 1602;	/ Is second source operand immediate?
1601:	R[rd] ← ADDCC(R[rs1],R[rs2]);	/ Perform ADDCC on register sources
	GOTO 2047;	
1602:	R[temp0] ← SEXT13(R[ir]);	/ Get sign extended simm13 field
1603:	R[rd] ← ADDCC(R[rs1],R[temp0]);	/ Perform ADDCC on register/simm13
	GOTO 2047;	/ sources
	/ andcc	
1604:	IF R[IR[13]] THEN GOTO 1606;	/ Is second source operand immediate?
1605:	R[rd] ← ANDCC(R[rs1],R[rs2]);	/ Perform ANDCC on register sources
	GOTO 2047;	
1606:	R[temp0] ← SIMM13(R[ir]);	/ Get simm13 field
1607:	R[rd] ← ANDCC(R[rs1],R[temp0]);	/ Perform ANDCC on register/simm13
	GOTO 2047;	/ sources
	/ orcc	
1608:	IF R[IR[13]] THEN GOTO 1610;	/ Is second source operand immediate?
1609:	R[rd] ← ORCC(R[rs1],R[rs2]);	/ Perform ORCC on register sources
	GOTO 2047;	
1610:	R[temp0] ← SIMM13(R[ir]);	/ Get simm13 field
1611:	R[rd] ← ORCC(R[rs1],R[temp0]);	/ Perform ORCC on register/simm13 sources
	GOTO 2047;	
	/ orncc	
1624:	IF R[IR[13]] THEN GOTO 1626;	/ Is second source operand immediate?
1625:	R[rd] ← NORCC(R[rs1],R[rs2]);	/ Perform ORNCC on register sources
	GOTO 2047;	
1626:	R[temp0] ← SIMM13(R[ir]);	/ Get simm13 field
1627:	R[rd] ← NORCC(R[rs1],R[temp0]);	/ Perform NORCC on register/simm13
	GOTO 2047;	/ sources
	/ srl	
1688:	IF R[IR[13]] THEN GOTO 1690;	/ Is second source operand immediate?
1689:	R[rd] ← SRL(R[rs1],R[rs2]);	/ Perform SRL on register sources
	GOTO 2047;	
1690:	R[temp0] ← SIMM13(R[ir]);	/ Get simm13 field
1691:	R[rd] ← SRL(R[rs1],R[temp0]);	/ Perform SRL on register/simm13 sources
	GOTO 2047;	
	/ jmp1	
1760:	IF R[IR[13]] THEN GOTO 1762;	/ Is second source operand immediate?
1761:	R[pc] ← ADD(R[rs1],R[rs2]);	/ Perform ADD on register sources
	GOTO 0;	

Partial ARC Microprogram (cont')


```

1762: R[temp0] ← SEXT13(R[ir]);           / Get sign extended simm13 field
1763: R[pc] ← ADD(R[rs1],R[temp0]);       / Perform ADD on register/simm13 sources
      GOTO 0;
      / ld
1792: R[temp0] ← ADD(R[rs1],R[rs2]);       / Compute source address
      IF R[IR[13]] THEN GOTO 1794;
1793: R[rd] ← AND(R[temp0],R[temp0]);     / Place source address on A bus
      READ; GOTO 2047;
1794: R[temp0] ← SEXT13(R[ir]);           / Get simm13 field for source address
1795: R[temp0] ← ADD(R[rs1],R[temp0]);     / Compute source address
      GOTO 1793;
      / st
1808: R[temp0] ← ADD(R[rs1],R[rs2]);       / Compute destination address
      IF R[IR[13]] THEN GOTO 1810;
1809: R[ir] ← RSHIFT5(R[ir]); GOTO 40;    / Move rd field into position of rs2 field
      40: R[ir] ← RSHIFT5(R[ir]);           / by shifting to the right by 25 bits.
      41: R[ir] ← RSHIFT5(R[ir]);
      42: R[ir] ← RSHIFT5(R[ir]);
      43: R[ir] ← RSHIFT5(R[ir]);
      44: R[0] ← AND(R[temp0], R[rs2]);     / Place destination address on A bus and
      WRITE; GOTO 2047;                   / place operand on B bus
1810: R[temp0] ← SEXT13(R[ir]);           / Get simm13 field for destination address
1811: R[temp0] ← ADD(R[rs1],R[temp0]);     / Compute destination address
      GOTO 1809;
      / Branch instructions: ba, be, bcs, bvs, bneg
1088: GOTO 2;                             / Decoding tree for branches
      2: R[temp0] ← LSHIFT10(R[ir]);       / Sign extend the 22 LSB's of %temp0
      3: R[temp0] ← RSHIFT5(R[temp0]);     / by shifting left 10 bits, then right 10
      4: R[temp0] ← RSHIFT5(R[temp0]);     / bits. RSHIFT5 does sign extension.
      5: R[ir] ← RSHIFT5(R[ir]);           / Move COND field to IR[13] by
      6: R[ir] ← RSHIFT5(R[ir]);           / applying RSHIFT5 three times. (The
      7: R[ir] ← RSHIFT5(R[ir]);           / sign extension is inconsequential.)
      8: IF R[IR[13]] THEN GOTO 12;       / Is it ba?
      R[ir] ← ADD(R[ir],R[ir]);
      9: IF R[IR[13]] THEN GOTO 13;       / Is it not be?
      R[ir] ← ADD(R[ir],R[ir]);
10: IF Z THEN GOTO 12;                    / Execute be
      R[ir] ← ADD(R[ir],R[ir]);
11: GOTO 2047;                             / Branch for be not taken
12: R[pc] ← ADD(R[pc],R[temp0]);         / Branch is taken
      GOTO 0;
13: IF R[IR[13]] THEN GOTO 16;           / Is it bcs?
      R[ir] ← ADD(R[ir],R[ir]);
14: IF C THEN GOTO 12;                    / Execute bcs
15: GOTO 2047;                             / Branch for bcs not taken
16: IF R[IR[13]] THEN GOTO 19;           / Is it bvs?
17: IF N THEN GOTO 12;                    / Execute bneg
18: GOTO 2047;                             / Branch for bneg not taken
19: IF V THEN GOTO 12;                    / Execute bvs
20: GOTO 2047;                             / Branch for bvs not taken
2047: R[pc] ← INCPC(R[pc]); GOTO 0;      / Increment %pc and start over

```

Branch Decoding

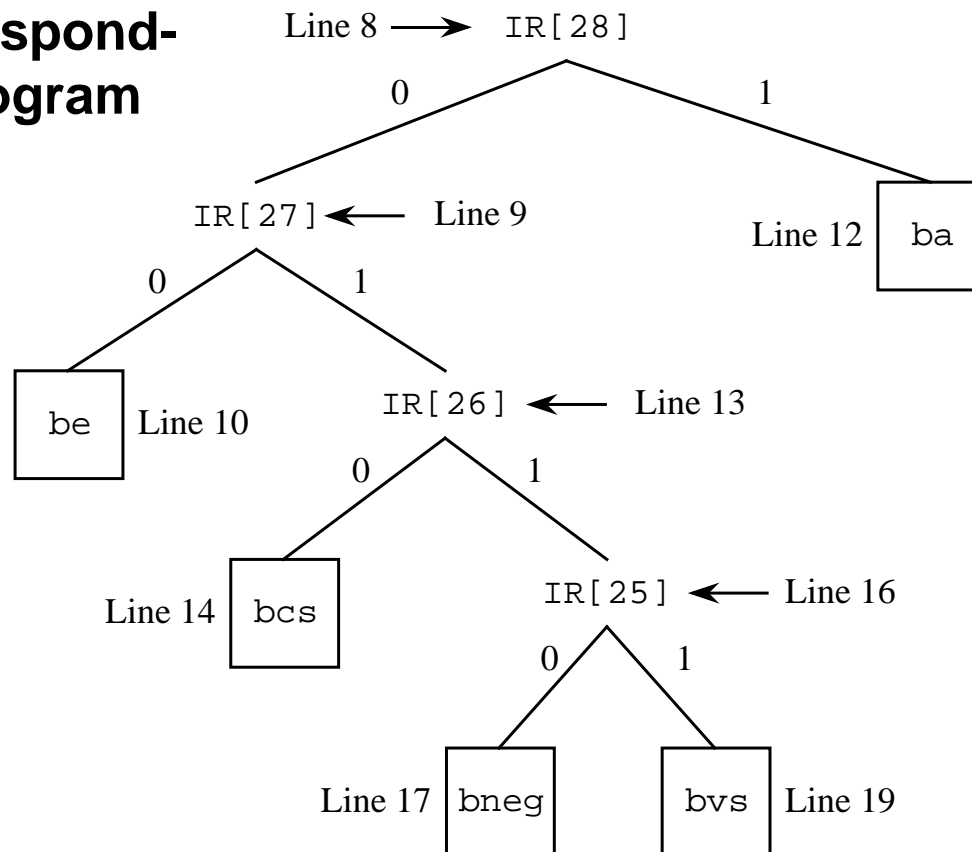- Decoding tree for branch instructions shows corresponding microprogram lines:



cond				branch
28	27	26	25	
0	0	0	1	be
0	1	0	1	bcs
0	1	1	0	bneg
0	1	1	1	bvs
1	0	0	0	ba

Assembled ARC Microprogram (cont')

	A	M	U	X	B	M	U	X	C	U	R	W	ALU	COND	JUMP	ADDR
	A	X	B	X	C	XDR	ALU	COND	JUMP	ADDR						
1793	1	0	0	0	0	1	0	1	0	0	0	0	0	0	1	1
1794	1	0	0	1	0	1	0	0	0	0	0	0	0	0	0	0
1795	0	0	0	0	0	1	1	0	0	0	0	1	0	0	0	0
1808	0	0	0	0	0	1	0	0	0	0	0	1	0	0	1	0
1809	1	0	0	1	0	1	0	0	0	0	0	1	1	1	1	1
40	1	0	0	1	0	1	0	0	0	0	0	1	1	1	1	1
41	1	0	0	1	0	1	0	0	0	0	0	1	1	1	1	1
42	1	0	0	1	0	1	0	0	0	0	0	1	1	1	1	1
43	1	0	0	1	0	1	0	0	0	0	0	1	1	1	1	1
44	1	0	0	0	1	0	0	0	0	0	1	0	1	0	1	1
1810	1	0	0	1	0	1	0	0	0	0	0	1	1	0	0	0
1811	0	0	0	0	0	1	1	0	0	0	1	0	0	0	1	1
1088	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1
2	1	0	0	1	0	1	0	0	0	0	0	1	0	1	0	0
3	1	0	0	0	1	0	0	0	0	0	0	1	1	1	1	1
4	1	0	0	0	1	0	0	0	0	0	0	1	1	1	1	1
5	1	0	0	1	0	1	0	0	0	0	0	1	1	1	1	1
6	1	0	0	1	0	1	0	0	0	0	0	1	1	1	1	1
7	1	0	0	1	0	1	0	0	0	0	0	1	1	1	1	1
8	1	0	0	1	0	1	0	0	1	0	0	1	0	0	0	1
9	1	0	0	1	0	1	0	0	1	0	0	1	0	0	0	1
10	1	0	0	1	0	1	0	0	1	0	0	1	0	0	0	1
11	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1
12	1	0	0	0	0	1	0	0	0	0	0	1	0	0	0	0
13	1	0	0	1	0	1	0	0	1	0	0	1	0	0	0	0
14	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1
15	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1
16	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1
17	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1
18	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1
19	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1
20	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	1
2047	1	0	0	0	0	0	0	0	0	0	0	1	1	1	0	1

Example: Add the subcc Instruction

- Consider adding instruction `subcc` (subtract) to the ARC instruction set. `subcc` uses the Arithmetic format and `op3 = 001100`.

```

1584: R[temp0] ← SEXT13(R[ir]);           / Extract rs2 operand
      IF IR[13] THEN GOTO 1586;           / Is second source immediate?
1585: R[temp0] ← R[rs2];                 / Extract sign extended immediate operand
1586: R[temp0] ← NOR(R[temp0], R[0]);     / Form one's complement of subtrahend
1587: R[temp0] ← INC(R[temp0]); GOTO 1603; / Form two's complement of subtrahend

```

	A	X	B	X	C	XDR	ALU	COND	JUMP	ADDR
1584	100101	00000000	00000000	0100001	000	1100	101	110001	10010	
1585	000000	00000000	1100001	000	000	1000	000	000000000000		
1586	100001	00000000	0100001	000	000	0111	000	000000000000		
1587	100001	00000000	0100001	000	000	1101	110	110010000011		


Branch Table

- A branch table for trap handlers and interrupt service routines:

Address	Contents	Trap Handler
	⋮	
60	JUMP TO 2000	Illegal instruction
64	JUMP TO 3000	Overflow
68	JUMP TO 3600	Underflow
72	JUMP TO 5224	Zerodivide
76	JUMP TO 4180	Disk
80	JUMP TO 5364	Printer
84	JUMP TO 5908	TTY
88	JUMP TO 6048	Timer
	⋮	

Microprogramming vs. Nanoprogramming

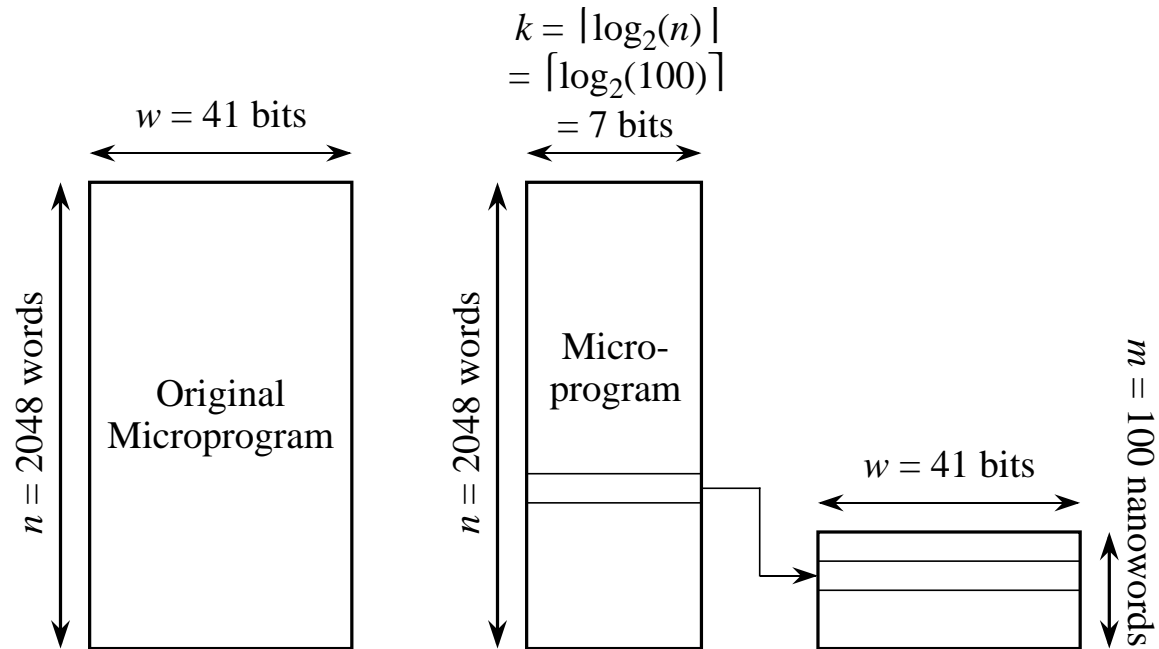- (a) Microprogramming vs. (b) nanoprogramming.



$$\text{Total Area} = n \times w = 2048 \times 41 = 83,968 \text{ bits}$$

$$\text{Microprogram Area} = n \times k = 2048 \times 7 = 14,336 \text{ bits}$$

$$\text{Nanoprogram Area} = m \times w = 100 \times 41 = 4100 \text{ bits}$$

$$\text{Total Area} = 14,336 + 4100 = 18,436 \text{ bits}$$

(a)

(b)

Hardware Description Language

- HDL sequence for a resettable modulo 4 counter.

```

Preamble {
MODULE: MOD_4_COUNTER.
INPUTS: x.
OUTPUTS: Z[2].
MEMORY:


Statements {
0: Z ← 0,0;
   GOTO {0 CONDITIONED ON x,
         1 CONDITIONED ON  $\bar{x}$ }.
1: Z ← 0,1;
   GOTO {0 CONDITIONED ON x,
         2 CONDITIONED ON  $\bar{x}$ }.
2: Z ← 1,0;
   GOTO {0 CONDITIONED ON x,
         3 CONDITIONED ON  $\bar{x}$ }.
3: Z ← 1,1;
   GOTO 0.

Epilogue {
END SEQUENCE.
END MOD_4_COUNTER.

```

Circuit Derived from HDL

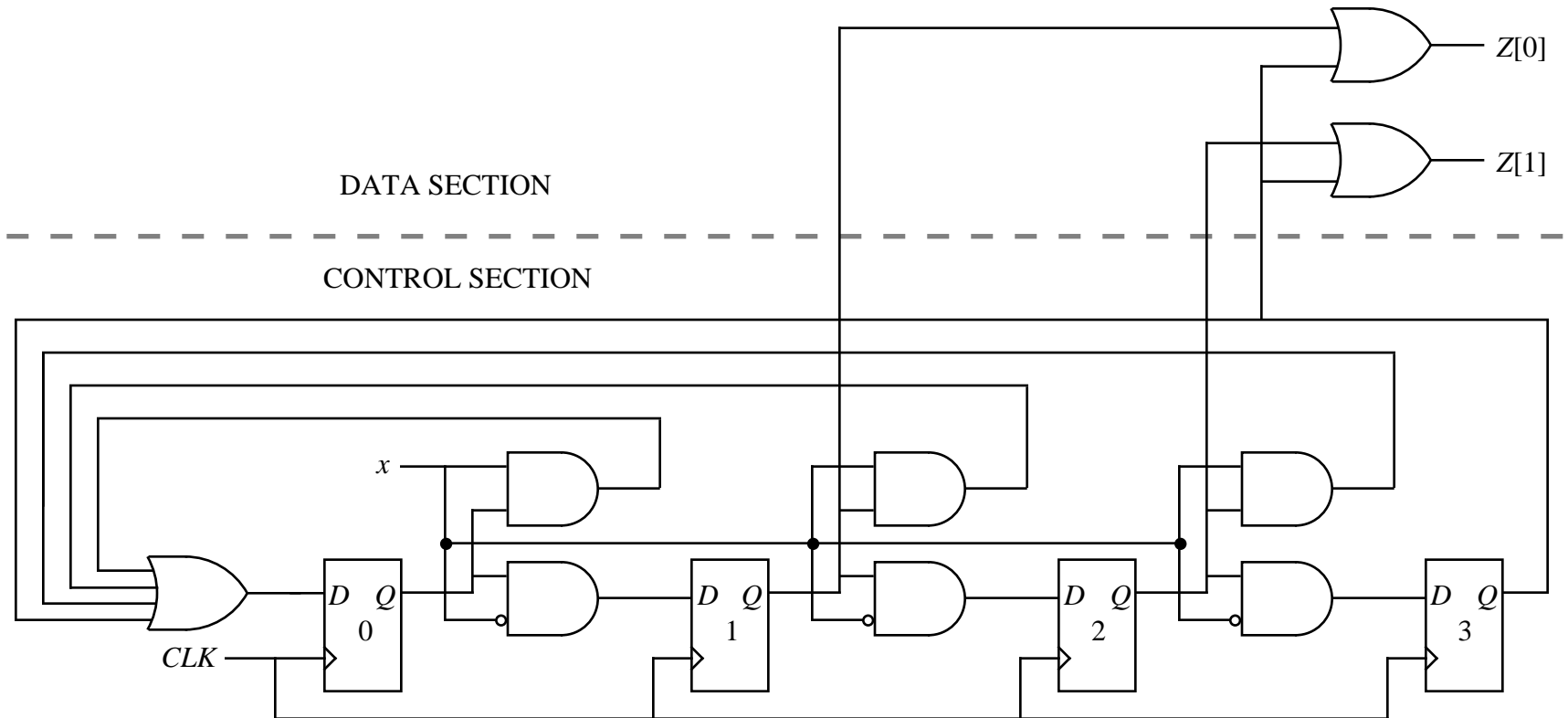- Logic design for a modulo 4 counter described in HDL.



HDL for ARC

- HDL description of the ARC control unit.

MODULE: ARC_CONTROL_UNIT.

INPUTS:

OUTPUTS: C, N, V, Z. ! These are set by the ALU

MEMORY: R[16][32], pc[32], ir[32], temp0[32], temp1[32], temp2[32],
temp3[32].

```

0: ir ← AND(pc, pc); Read ← 1;           ! Instruction fetch
    ! Decode op field
1: GOTO {2 CONDITIONED ON ir[31]×ir[30], ! Branch/sethi format: op=00
        4 CONDITIONED ON ir[31]×ir[30], ! Call format: op=01
        8 CONDITIONED ON ir[31]×ir[30], ! Arithmetic format: op=10
        10 CONDITIONED ON ir[31]×ir[30]}. ! Memory format: op=11
    ! Decode op2 field
2: GOTO 19 CONDITIONED ON ir[24].       ! Goto 19 if Branch format
3: R[rd] ← ir[imm22];                   ! sethi
    GOTO 20.
4: R[15] ← AND(pc, pc).                 ! call: save pc in register 15
5: temp0 ← ADD(ir, ir).                 ! Shift disp30 field left
6: temp0 ← ADD(ir, ir).                 ! Shift again
7: pc ← ADD(pc, temp0); GOTO 0.         ! Jump to subroutine
    ! Get second source operand into temp0 for Arithmetic format
8: temp0 ← { SEXT13(ir) CONDITIONED ON ir[13]×NOR(ir[19:22]), ! addcc
R[rs2] CONDITIONED ON ir[13]×NOR(ir[19:22]), ! addcc
SIMM13(ir) CONDITIONED ON ir[13]×OR(ir[19:22]), ! Remaining
R[rs2] CONDITIONED ON ir[13]×OR(ir[19:22])}. ! Arithmetic instructions
    ! Decode op3 field for Arithmetic format
9: R[rd] ← {
    ADDCC(R[rs1], temp0) CONDITIONED ON XNOR(IR[19:24], 010000), ! addcc
    ANDCC(R[rs1], temp0) CONDITIONED ON XNOR(IR[19:24], 010001), ! andcc
    ORCC(R[rs1], temp0) CONDITIONED ON XNOR(IR[19:24], 010010), ! orcc
    NORCC(R[rs1], temp0) CONDITIONED ON XNOR(IR[19:24], 010110), ! ornc
    SRL(R[rs1], temp0) CONDITIONED ON XNOR(IR[19:24], 100110), ! srl
    ADD(R[rs1], temp0) CONDITIONED ON XNOR(IR[19:24], 111000)}; ! jmp1
    GOTO 20.
    ! Get second source operand into temp0 for Memory format
10: temp0 ← {SEXT13(ir) CONDITIONED ON ir[13],
R[rs2] CONDITIONED ON ir[13]}.
11: temp0 ← ADD(R[rs1], temp0).
    ! Decode op3 field for Memory format
    GOTO {12 CONDITIONED ON ir[21], ! ld
        13 CONDITIONED ON ir[21]}. ! st
12: R[rd] ← AND(temp0, temp0); Read ← 1; GOTO 20.
13: ir ← RSHIFT5(ir).

```

HDL for ARC (cont')


```

14: ir ← RSHIFT5(ir).
15: ir ← RSHIFT5(ir).
16: ir ← RSHIFT5(ir).
17: ir ← RSHIFT5(ir).
18: r0 ← AND(temp0, R[rs2]); Write ← 1; GOTO 20.
19: pc ← { ! Branch instructions
      ADD(pc, temp0) CONDITIONED ON ir[28] + ir[28]×ir[27]×Z +
        ir[28]×ir[27]×ir[26]×C + ir[28]×ir[27]×ir[26]×ir[25]×N +
        ir[28]×ir[27]×ir[26]×ir[25]×V,
      INCPC(pc) CONDITIONED ON ir[28]×ir[27]×Z +
        ir[28]×ir[27]×ir[26]×C + ir[28]×ir[27]×ir[26]×ir[25]×N +
        ir[28]×ir[27]×ir[26]×ir[25]×V};
      GOTO 0.
20: pc ← INCPC(pc); GOTO 0.
END SEQUENCE.
END ARC_CONTROL_UNIT.

```


HDL ARC Circuit

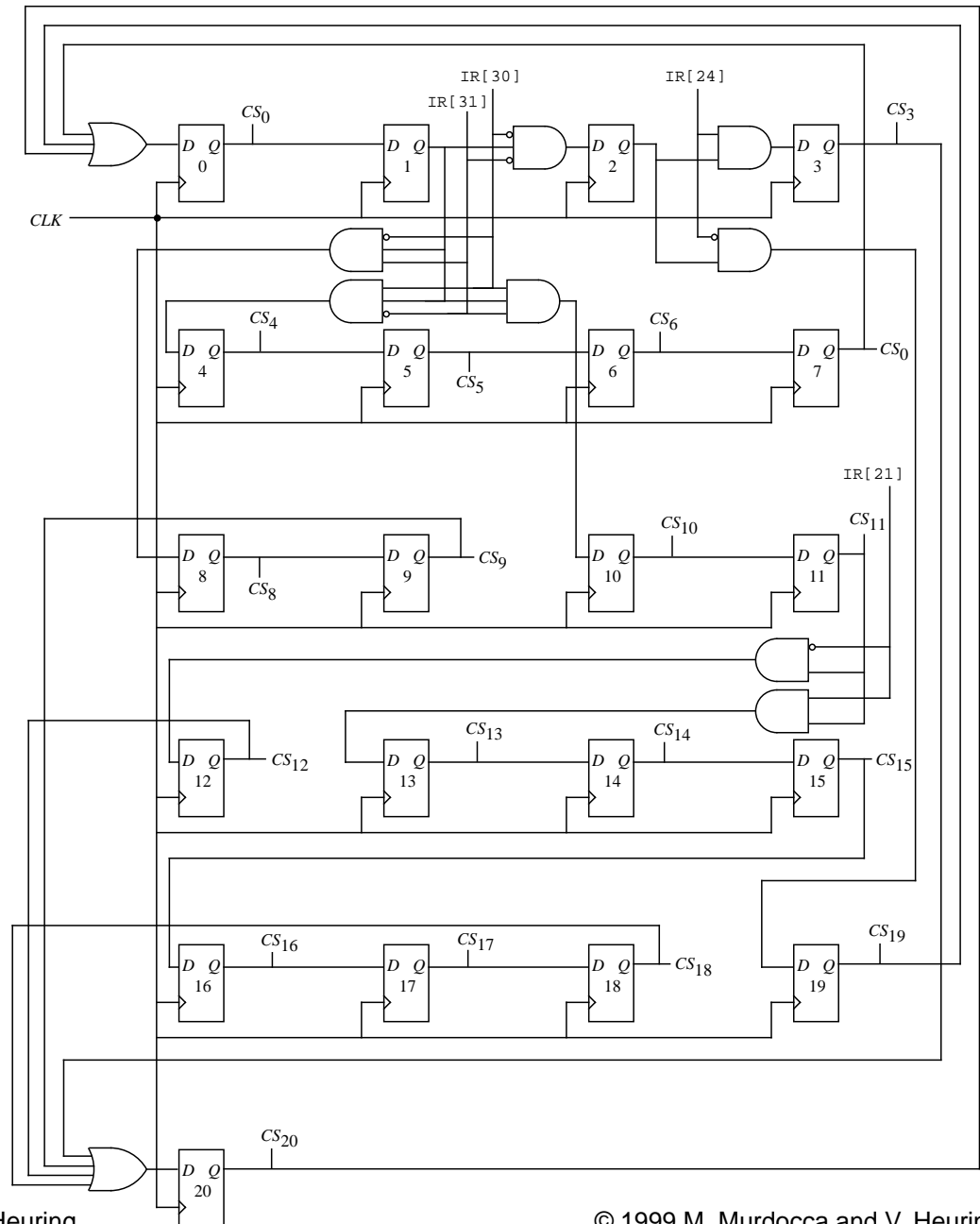- The hardwired control section of the ARC: generation of the control signals.



HDL ARC Circuit (cont')

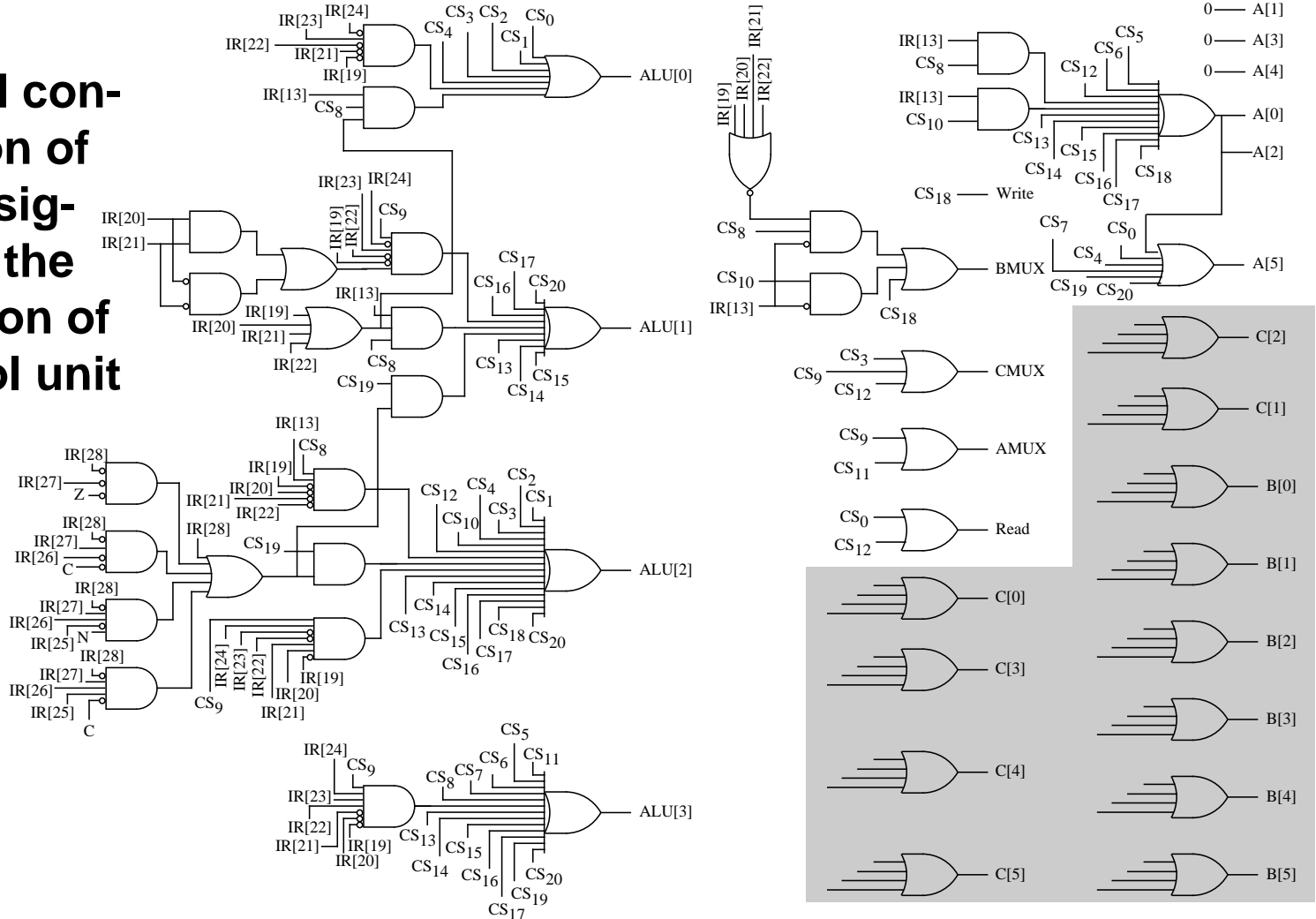- **Hardwired control section of the ARC: signals from the data section of the control unit to the datapath.**




Case Study: The VHDL Hardware Description Language


- The majority function. a) truth table, b) AND-OR implementation, c) black box representation.

Minterm Index	A	B	C	F
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1

a)

 

b)

 

c)

VHDL Specification

Interface specification for the majority component

```
-- Interface
entity MAJORITY is
  port
    (A_IN, B_IN, C_IN: in BIT
     F_OUT: out BIT);
end MAJORITY;
```

Behavioral model for the majority component

```
-- Body
architecture LOGIC_SPEC of MAJORITY is
begin
  -- compute the output using a Boolean expression
  F_OUT      <= (not A_IN and B_IN and C_IN) or
                (A_IN and not B_IN and C_IN) or
                (A_IN and B_IN and not C_IN) or
                (A_IN and B_IN and C_IN) after 4 ns;
end LOGIC_SPEC;
```

VHDL Specification (cont')

```
-- Package declaration, in library WORK
package LOGIC_GATES is
component AND3
    port (A, B, C : in BIT; X : out BIT);
end component;
component OR4
    port (A, B, C, D : in BIT; X : out BIT);
end component;
component NOT1
    port (A : in BIT; X : out BIT);
end component;

-- Interface
entity MAJORITY is
    port
        (A_IN, B_IN, C_IN: in BIT
         F_OUT: out BIT);
end MAJORITY;
```

VHDL Specification (cont')

```
-- Body
-- Uses components declared in package LOGIC_GATES
-- in the WORK library
-- import all the components in WORK.LOGIC_GATES
use WORK.LOGIC_GATES.all
architecture LOGIC_SPEC of MAJORITY is
-- declare signals used internally in MAJORITY
signal A_BAR, B_BAR, C_BAR, I1, I2, I3, I4: BIT;
begin
-- connect the logic gates
NOT_1 : NOT1 port map (A_IN, A_BAR);
NOT_2 : NOT1 port map (B_IN, B_BAR);
NOT_3 : NOT1 port map (C_IN, C_BAR);
AND_1 : AND3 port map (A_BAR, B_IN, C_IN, I1);
AND_2 : AND3 port map (A_IN, B_BAR, C_IN, I2);
AND_3 : AND3 port map (A_IN, B_IN, C_BAR, I3);
AND_4 : AND3 port map (A_IN, B_IN, C_IN, I4);
OR_1 : OR3 port map (I1, I2, I3, I4, F_OUT);
end LOGIC_SPEC;
```